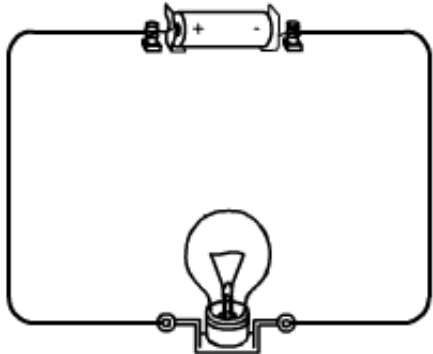
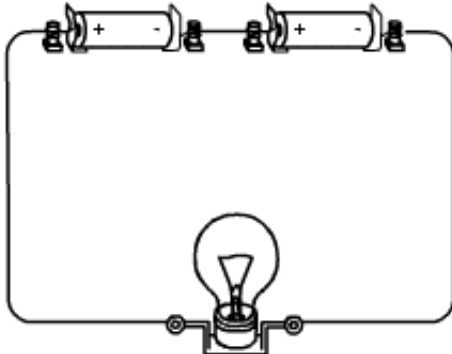


Circuits and conductors

Name.....

Write in the space below each of the circuits whether the bulb or bulbs would be a) off, b) glowing dimly, c) glowing normally or d) glowing brightly. The first one has been done for you.

	
<p>Glowing normally</p>	
